

# Resistance Lab

**Vincent Edwards, Ali Mortada, Andrew Bringas**

Mt. San Antonio College, Physics 4B, CRN 42240  
April 26, 2023

## 1. Purpose

For part 1, the goal was to examine how material, cross-sectional area, and length impact resistance. For each coil of wire, resistance was determined in three ways: based on measurements of voltage and current; based on the resistance readings from the multimeter; and based on the dimensions of the wires and the resistivity of the materials. In addition, the results of the three methods of determining resistance were compared.

## 2. Results

Table 1 contains the properties of the resistance coils used in part 1.  $\rho$  is the resistivity of the material.  $L$  is the length of the coil of wire.  $D$  is the diameter of the wire. The values for  $\rho$ ,  $L$ , and  $D$  were assumed to be exact, without uncertainty. In addition, note that Nickel-Silver is a copper alloy consisting of copper, nickel, and zinc or manganese. The exact composition of the alloy used in the experiment is unknown. Thus, the resistivity was approximated to be  $44 \times 10^{-8} \Omega \text{ m}$ , the value for Manganin (Cu 84%, Mn 12%, Ni 4%), an alloy of similar composition.

**Table 1.** Part 1 Resistance Coils

Coil	Material	$\rho$ ( $\Omega \text{ m}$ )	$L$ (cm)	$D$ (cm)
1	Nickel-Silver	$44 \times 10^{-8}$	40	0.0254
2	Nickel-Silver	$44 \times 10^{-8}$	80	0.0254
3	Nickel-Silver	$44 \times 10^{-8}$	120	0.0254
4	Nickel-Silver	$44 \times 10^{-8}$	160	0.0254
5	Nickel-Silver	$44 \times 10^{-8}$	200	0.0254
6	Nickel-Silver	$44 \times 10^{-8}$	200	0.0320
7	Copper	$1.72 \times 10^{-8}$	2000	0.0254

Table 2 contains the measurements made during part 1.  $V$  is the voltage across the resistance coil.  $I$  is the current through the resistance coil.  $(R_m + r)$  is the resistance, measured using the multimeter, of the resistance coil and the wires connecting it to the multimeter.  $r$  is the resistance, measured using the multimeter to be  $0.1 \pm 0.1 \Omega$ , of just the wires used for connecting the multimeter to the resistance coil.

Table 3 contains the two experimental values for resistance in the coil ( $R_{V/I}$  and  $R_m$ ) and the theoretical value ( $R_{th}$ ).  $R_{V/I}$  is the experimental resistance determined using the measured values for  $V$  and  $I$ .  $R_m$  is the experimental resistance determined using the readings from the multimeter.  $R_{th}$  is the theoretical resistance determined using the dimensions of the wires ( $L$  and  $D$ ) and the resistivity of the material ( $\rho$ ).

Figure 1 plots resistance ( $R_{V/I}$ ,  $R_m$ , and  $R_{th}$ ) versus length ( $L$ ) for the first five resistance coils used in part 1. Those coils were chosen for the graph as they all had the same material and diameter. Since the graphs seemed linear (and that's what theory predicts) a linear fit was applied.

**Table 2.** Part 1 Measurements

Note:  $r$ , the resistance of the two wires connected to the multimeter, was measured to be  $0.1 \pm 0.1 \, \Omega$ .

Coil	$V$ (V)	$I$ (mA)	$R_m + r$ ( $\Omega$ )
1	$0.214 \pm 0.001$	$55.07 \pm 0.05$	$4.0 \pm 0.1$
2	$0.400 \pm 0.001$	$49.72 \pm 0.01$	$8.3 \pm 0.1$
3	$0.536 \pm 0.001$	$44.53 \pm 0.02$	$12.0 \pm 0.1$
4	$0.662 \pm 0.001$	$41.70 \pm 0.01$	$15.9 \pm 0.1$
5	$0.772 \pm 0.001$	$38.19 \pm 0.01$	$20.3 \pm 0.1$
6	$0.538 \pm 0.001$	$45.44 \pm 0.01$	$11.7 \pm 0.1$
7	$0.357 \pm 0.001$	$51.31 \pm 0.01$	$7.3 \pm 0.1$

**Table 3.** Part 1 Experimental and Theoretical Resistances

Coil	$R_{V/I}$ ( $\Omega$ )	$R_m$ ( $\Omega$ )	$R_{th}$ ( $\Omega$ )
1	$3.89 \pm 0.02$	$3.9 \pm 0.1$	3.47
2	$8.05 \pm 0.02$	$8.2 \pm 0.1$	6.95
3	$12.04 \pm 0.02$	$11.9 \pm 0.1$	10.42
4	$15.88 \pm 0.02$	$15.8 \pm 0.1$	13.89
5	$20.21 \pm 0.03$	$20.2 \pm 0.1$	17.37
6	$11.84 \pm 0.02$	$11.6 \pm 0.1$	10.94
7	$6.96 \pm 0.02$	$7.2 \pm 0.1$	6.79

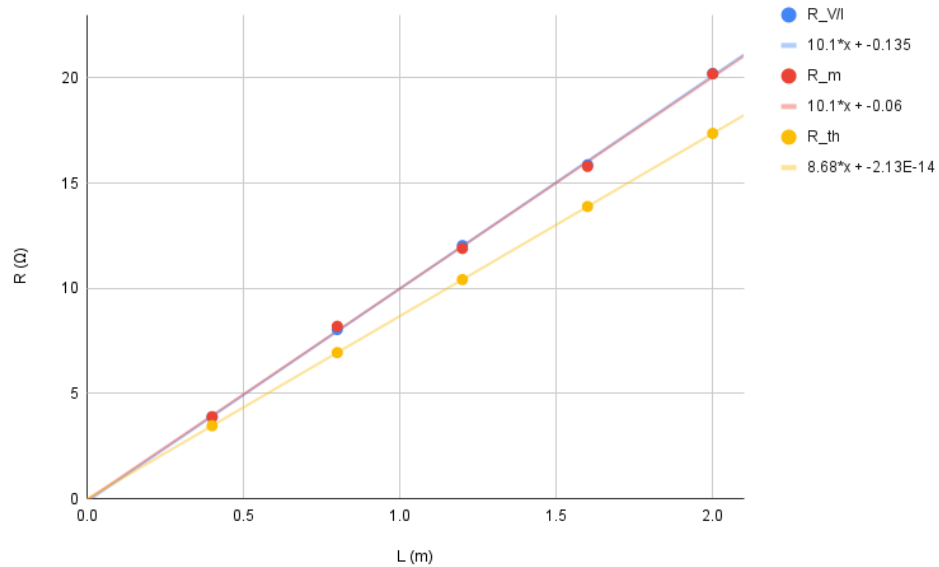
**Figure 1.** Resistance vs Length (Constant  $\rho$  and  $A$ )

Table 4 contains the resistances measured using a multimeter of the two nichrome resistors used in part 2.  $(R + r)$  is the resistance, measured using the multimeter, of the nichrome resistor and the wires connecting it to the multimeter.  $r$  is the resistance, measured using the multimeter to be  $0.9 \pm 0.1 \, \Omega$ , of just the wires used for connecting the multimeter to the nichrome resistor.  $R$  is the calculated resistance of the nichrome resistor based on these measurements. These resistance values,  $R_1 = 11.4 \pm 0.1 \, \Omega$  and  $R_2 = 29.7 \pm 0.1 \, \Omega$ , will be referred to as the true values.

**Table 4.** Part 2 True Resistances

Note:  $r$ , the resistance of the two wires connected to the multimeter, was measured to be  $0.9 \pm 0.1 \, \Omega$ .

	$R + r \, (\Omega)$	$R \, (\Omega)$
1	$12.3 \pm 0.1$	$11.4 \pm 0.1$
2	$30.6 \pm 0.1$	$29.7 \pm 0.1$

Table 5 contains the values for the circuit with just  $R_1$  connected to the power supply.  $V$  is the voltage across the nichrome resistor.  $I$  is the current through the nichrome resistor.  $R_{V/I}$  is the experimental resistance determined using the measured values for  $V$  and  $I$ .

**Table 5.** Part 2  $R_1$  Experimental Values

$V \, (\text{V})$	$I \, (\text{mA})$	$R_{V/I} \, (\Omega)$
$0.000 \pm 0.001$	$0.00 \pm 0.01$	undefined
$0.744 \pm 0.001$	$66.8 \pm 0.1$	$11.14 \pm 0.02$
$1.491 \pm 0.001$	$134.0 \pm 0.1$	$11.13 \pm 0.01$
$2.257 \pm 0.001$	$202.8 \pm 0.1$	$11.129 \pm 0.007$
$3.0 \pm 0.001$	$269.6 \pm 0.1$	$11.128 \pm 0.006$

Table 6 contains the values for the circuit with just  $R_2$  connected to the power supply.  $V$  is the voltage across the nichrome resistor.  $I$  is the current through the nichrome resistor.  $R_{V/I}$  is the experimental resistance determined using the measured values for  $V$  and  $I$ .

**Table 6.** Part 2  $R_2$  Experimental Values

$V \, (\text{V})$	$I \, (\text{mA})$	$R_{V/I} \, (\Omega)$
$0.000 \pm 0.001$	$0.00 \pm 0.01$	undefined
$0.746 \pm 0.001$	$24.96 \pm 0.01$	$29.89 \pm 0.04$
$1.500 \pm 0.001$	$50.16 \pm 0.01$	$29.9 \pm 0.02$
$2.255 \pm 0.001$	$75.4 \pm 0.1$	$29.91 \pm 0.04$
$2.998 \pm 0.001$	$100.3 \pm 0.1$	$29.89 \pm 0.03$

Table 7 contains the values for the circuit with  $R_1$  and  $R_2$  connected to the power supply in series.  $V$  is the voltage across both nichrome resistors.  $I$  is the current through both nichrome resistors.  $R_{V/I}$  is the experimental resistance determined using the measured values for  $V$  and  $I$ .

**Table 7.** Part 2  $R_{1+2}$  Experimental Values

$V$ (V)	$I$ (mA)	$R_{V/I}$ ( $\Omega$ )
$0.000 \pm 0.001$	$0.00 \pm 0.01$	undefined
$0.757 \pm 0.001$	$18.37 \pm 0.01$	$41.21 \pm 0.06$
$1.496 \pm 0.001$	$36.29 \pm 0.01$	$41.22 \pm 0.03$
$2.254 \pm 0.001$	$54.69 \pm 0.01$	$41.21 \pm 0.02$
$3.001 \pm 0.001$	$72.8 \pm 0.1$	$41.22 \pm 0.06$

Table 8 contains the values for the circuit with  $R_1$  and  $R_2$  connected to the power supply in parallel.  $V$  is the voltage across both nichrome resistors.  $I$  is the current through both nichrome resistors.  $R_{V/I}$  is the experimental resistance determined using the measured values for  $V$  and  $I$ .

**Table 8.** Part 2  $R_{1||2}$  Experimental Values

$V$ (V)	$I$ (mA)	$R_{V/I}$ ( $\Omega$ )
$0.000 \pm 0.001$	$0.00 \pm 0.01$	undefined
$0.749 \pm 0.001$	$91.4 \pm 0.1$	$8.19 \pm 0.01$
$1.502 \pm 0.001$	$183.5 \pm 0.1$	$8.185 \pm 0.007$
$2.252 \pm 0.001$	$275.5 \pm 0.1$	$8.174 \pm 0.005$
$3.000 \pm 0.001$	$367.6 \pm 0.1$	$8.161 \pm 0.004$

Table 9 contains the voltage and current measurements made of the series circuit at 4 V.  $V_1$  is the voltage across resistor 1.  $V_2$  is the voltage across resistor 2.  $V_{1+2}$  is the voltage across both resistors.  $I_1$  is the current between the resistors, after coming from the power supply and through resistor 1.  $I_2$  is the current after resistor 2, right before reaching the negative terminal of the power supply.  $I_{1+2}$  is the current next to the positive terminal of the power supply, right before reaching the first resistor.

**Table 9.** Part 2 Series Circuit at 4 V

	$V$ (V)	$I$ (mA)
$R_1$	$1.084 \pm 0.001$	$96.5 \pm 0.1$
$R_2$	$2.915 \pm 0.001$	$97.1 \pm 0.1$
$R_{1+2}$	$4.002 \pm 0.001$	$97.1 \pm 0.1$

Table 10 contains the voltage and current measurements made of the parallel circuit at 4 V.  $V_1$  is the voltage across resistor 1.  $V_2$  is the voltage across resistor 2.  $V_{1||2}$  is

the voltage across both resistors.  $I_1$  is the current through resistor 1.  $I_2$  is the current through resistor 2.  $I_{1||2}$  is the current next to the positive terminal of the power supply, right before reaching the junction connected to the two resistors.

**Table 10.** Part 2 Parallel Circuit at 4 V

	$V$ (V)	$I$ (mA)
$R_1$	$3.968 \pm 0.001$	$410.4 \pm 0.1$
$R_2$	$3.927 \pm 0.001$	$155.6 \pm 0.1$
$R_{1  2}$	$4.002 \pm 0.001$	$491.7 \pm 0.1$

### 3. Uncertainty

All the voltage, current, and resistance measurements in the experiment were made using a multimeter. If there were fluctuations in a particular reading with the multimeter (voltage, current, or resistance), then the uncertainty was taken to be the magnitude of the fluctuations, as that gives an upper bound for how much the value could have varied. If the reading with the multimeter (voltage, current, or resistance) was stable and did not fluctuate, then the uncertainty was taken to be the smallest increment of measure, since that was the limiting precision of the equipment.

In part 1,  $R_{V/I}$  was calculated using equation 1.

$$R_{V/I} = \frac{V}{I} \quad (1)$$

The uncertainty of  $R_{V/I}$  is given by equation 2.

$$\begin{aligned} \Delta R_{V/I} &= \left[ \left( \frac{\partial R_{V/I}}{\partial V} \Delta V \right)^2 + \left( \frac{\partial R_{V/I}}{\partial I} \Delta I \right)^2 \right]^{\frac{1}{2}} \\ &= \frac{V}{I} \left[ \left( \frac{\Delta V}{V} \right)^2 + \left( \frac{\Delta I}{I} \right)^2 \right]^{\frac{1}{2}} \end{aligned} \quad (2)$$

In part 1,  $R_m$  was calculated using equation 3. Note that the combined value ( $R_m + r$ ) was measured, as was the value for  $r$ . But  $R_m$  was not measured, hence why it is being calculated as a difference of two values.

$$R_m = (R_m + r) - r \quad (3)$$

The uncertainty of  $R_m$  is given by equation 4.

$$\begin{aligned} \Delta R_m &= \left[ \left( \frac{\partial R_m}{\partial (R_m + r)} \Delta (R_m + r) \right)^2 + \left( \frac{\partial R_m}{\partial r} \Delta r \right)^2 \right]^{\frac{1}{2}} \\ &= \left[ (\Delta (R_m + r))^2 + (\Delta r)^2 \right]^{\frac{1}{2}} \end{aligned} \quad (4)$$

In part 1,  $R_{\text{th}}$  was calculated using equation 5.

$$\begin{aligned} R_{\text{th}} &= \frac{\rho L}{A} \\ &= \frac{\rho L}{\pi(D/2)^2} \\ &= \frac{4\rho L}{\pi D^2} \end{aligned} \tag{5}$$

Note that the values for  $\rho$ ,  $L$ , and  $D$  were assumed to be exact, without uncertainty. Thus,  $R_{\text{th}}$  would have no uncertainty as well.

#### 4. Conclusion

In part 1, the resistances of 7 different resistance coils were determined using three different techniques. Descriptions of the coils are in table 1, and the calculated resistance values are in table 3. The experimental resistances  $R_{V/I}$  and  $R_m$  had similar values for all the coils. Coils 1, 4, and 5 had resistance values that overlapped within uncertainty, while the rest of the coils (2, 3, 6, and 7) had values that were still fairly close and almost within uncertainty. While the experimental resistances were similar, their values were all higher than the corresponding theoretical resistances  $R_{\text{th}}$ . One possible explanation is that when measuring voltage and resistance, the multimeter was connected to the resistance coils through a small bit of copper wire. This copper wire section was not included when measuring  $r$ , but it was included when measuring  $(R_m + r)$ . As a result, this would cause  $R_m$  to be higher than expected. This extra resistance would also have increased the measured value for  $V$ , thereby causing  $R_{V/I}$  to be higher than expected. Another possibility is that the temperature of the room did not match the reference temperature of 20 °C. The table the resistivity values were taken from used a reference temperature of 20 °C. If the room were warmer than 20 °C, then the actual resistivity values would have been slightly higher than the  $\rho$  values used for calculations. This would cause  $R_{\text{th}}$  to be lower than expected.

Resistance coils 1 through 5 were all made of the same material and had the same cross-sectional area, but they had different lengths. Figure 1 plots resistance ( $R_{V/I}$ ,  $R_m$ , and  $R_{\text{th}}$ ) versus length ( $L$ ). The graphs are linear with y-intercepts close to zero. Thus, the data indicates that the resistance of a wire/coil is proportional to its length.

Resistance coils 5 and 6 were made of the same material and had the same length, but they had different cross-sectional areas. The experimental resistances for coil 5 ( $R_{V/I} = 20.21 \pm 0.03 \, \Omega$ ,  $R_m = 20.2 \pm 0.1 \, \Omega$ ) were higher than the experimental resistances for coil 6 ( $R_{V/I} = 11.84 \pm 0.02 \, \Omega$ ,  $R_m = 11.6 \pm 0.1 \, \Omega$ ). The cross-sectional area of coil 5 ( $A = \frac{1}{4}\pi(0.0254 \, \text{cm})^2 = 5.07 \times 10^{-4} \, \text{cm}^2$ ) was lower than the cross-sectional area of coil 6 ( $A = \frac{1}{4}\pi(0.0320 \, \text{cm})^2 = 8.04 \times 10^{-4} \, \text{cm}^2$ ). Thus, the data suggests that as cross-sectional area increases, resistances decreases.

Resistance coil 7, made out of copper, was 10 times longer than coil 5, made out of nickel-silver, with the same cross-sectional area. Since it has already been shown that

resistance is proportional to length, then dividing the experimental resistance values for coil 7 by 10 would allow us to compare the resistances of two wires of identical dimensions but different materials. Thus, our hypothetical 200 cm long copper resistance coil of diameter 0.0254 cm would have experimental resistances  $R_{V/I} = 0.696 \pm 0.002 \, \Omega$  and  $R_m = 0.72 \pm 0.01 \, \Omega$ . For comparison, coil 5 had experimental resistances  $R_{V/I} = 20.21 \pm 0.03 \, \Omega$  and  $R_m = 20.2 \pm 0.1 \, \Omega$ . The resistance of coil 5 was much higher than the resistance of the hypothetical copper wire with identical length and diameter. This supports the idea that resistance depends on material, with some materials having more resistance for a given wire shape than others.

## 5. Citations

- [1] Karen Schnurbusch, *Physics 4B Lab Book*, Mt. San Antonio College, 2023, pp. 65-70.
- [2] Karen Schnurbusch, *Physics 4B Equations*, Mt. San Antonio College, 2023, pp. 4, 10.