

# Circuits Lab

**Vincent Edwards**

Mt. San Antonio College, Physics 4B, CRN 42240  
May 8, 2023

$$R_2 = 40 \, \Omega$$

## **1. Purpose**

The goal of the exercise was to use Kirchhoff's rules to analyze 7 different circuits and calculate current, voltage, and power for each circuit element. For the first 4 circuits, the voltage and current calculations were compared to results obtained using an online circuit simulator.

## **2. Results**

## **3. Conclusion**

## **4. Citations**

- [1] Karen Schnurbusch, *Physics 4B Lab Book*, Mt. San Antonio College, 2023, pp. 71-74.
- [2] Karen Schnurbusch, *Physics 4B Equations*, Mt. San Antonio College, 2023, pp. 4, 5.