

# Resistance Lab

**Vincent Edwards, Ali Mortada, Andrew Bringas**

Mt. San Antonio College, Physics 4B, CRN 42240  
April 26, 2023

## 1. Purpose

For part 1, the goal was to examine how material, cross-sectional area, and length impact resistance. For each coil of wire, resistance was determined in three ways: based on measurements of voltage and current, based on the resistance readings from the multimeter, and based on the dimensions of the wires and the resistivity of the materials. The results of the three methods of determining resistance were compared.

For part 2, the goal was to examine voltage, current, and resistance for two resistors in series and two resistors in parallel. For each nichrome resistor, resistance was determined in two ways: based on measurements of voltage and current, and based on the resistance readings from the multimeter. The results of these two methods were compared. The readings from the multimeter were accepted as the true resistance values, which were then used to calculate the theoretical resistance of the resistors in series and the resistors in parallel. These theoretical resistances were compared to experimental values found by setting up the circuits and measuring voltage and current. In addition, measurements of voltage and current were made at different parts of the series and parallel circuits in order to see if they matched what theory predicts.

## 2. Results

Table 1 contains the properties of the resistance coils used in part 1.  $\rho$  is the resistivity of the material.  $L$  is the length of the coil of wire.  $D$  is the diameter of the wire. The values for  $\rho$ ,  $L$ , and  $D$  were assumed to be exact, without uncertainty. In addition, note that Nickel-Silver is a copper alloy consisting of copper, nickel, and zinc or manganese. The exact composition of the alloy used in the experiment is unknown. Thus, the resistivity was approximated to be  $44 \times 10^{-8} \Omega \text{ m}$ , the value for Manganin (Cu 84%, Mn 12%, Ni 4%), an alloy of similar composition.

**Table 1.** Part 1 Resistance Coils

Coil	Material	$\rho$ ( $\Omega \text{ m}$ )	$L$ (cm)	$D$ (cm)
1	Nickel-Silver	$44 \times 10^{-8}$	40	0.0254
2	Nickel-Silver	$44 \times 10^{-8}$	80	0.0254
3	Nickel-Silver	$44 \times 10^{-8}$	120	0.0254
4	Nickel-Silver	$44 \times 10^{-8}$	160	0.0254
5	Nickel-Silver	$44 \times 10^{-8}$	200	0.0254
6	Nickel-Silver	$44 \times 10^{-8}$	200	0.0320
7	Copper	$1.72 \times 10^{-8}$	2000	0.0254

Table 2 contains the measurements made during part 1.  $V$  is the voltage across the resistance coil.  $I$  is the current through the resistance coil.  $(R_m + r)$  is the resistance, measured using the multimeter, of the resistance coil and the wires connecting it to the multimeter.  $r$  is the resistance, measured using the multimeter to be  $0.1 \pm 0.1 \Omega$ , of just the wires used for connecting the multimeter to the resistance coil.

**Table 2.** Part 1 Measurements

Note:  $r$ , the resistance of the two wires connected to the multimeter, was measured to be  $0.1 \pm 0.1 \, \Omega$ .

Coil	$V$ (V)	$I$ (mA)	$R_m + r$ ( $\Omega$ )
1	$0.214 \pm 0.001$	$55.07 \pm 0.05$	$4.0 \pm 0.1$
2	$0.400 \pm 0.001$	$49.72 \pm 0.01$	$8.3 \pm 0.1$
3	$0.536 \pm 0.001$	$44.53 \pm 0.02$	$12.0 \pm 0.1$
4	$0.662 \pm 0.001$	$41.70 \pm 0.01$	$15.9 \pm 0.1$
5	$0.772 \pm 0.001$	$38.19 \pm 0.01$	$20.3 \pm 0.1$
6	$0.538 \pm 0.001$	$45.44 \pm 0.01$	$11.7 \pm 0.1$
7	$0.357 \pm 0.001$	$51.31 \pm 0.01$	$7.3 \pm 0.1$

Table 3 contains the two experimental values for resistance in the coil ( $R_{V/I}$  and  $R_m$ ) and the theoretical value ( $R_{th}$ ).  $R_{V/I}$  is the experimental resistance determined using the measured values for  $V$  and  $I$ .  $R_m$  is the experimental resistance determined using the readings from the multimeter.  $R_{th}$  is the theoretical resistance determined using the dimensions of the wires ( $L$  and  $D$ ) and the resistivity of the material ( $\rho$ ).


**Table 3.** Part 1 Experimental and Theoretical Resistances

Coil	$R_{V/I}$ ( $\Omega$ )	$R_m$ ( $\Omega$ )	$R_{th}$ ( $\Omega$ )
1	$3.89 \pm 0.02$	$3.9 \pm 0.1$	3.47
2	$8.05 \pm 0.02$	$8.2 \pm 0.1$	6.95
3	$12.04 \pm 0.02$	$11.9 \pm 0.1$	10.42
4	$15.88 \pm 0.02$	$15.8 \pm 0.1$	13.89
5	$20.21 \pm 0.03$	$20.2 \pm 0.1$	17.37
6	$11.84 \pm 0.02$	$11.6 \pm 0.1$	10.94
7	$6.96 \pm 0.02$	$7.2 \pm 0.1$	6.79

Figure 1 plots resistance ( $R_{V/I}$ ,  $R_m$ , and  $R_{th}$ ) versus length ( $L$ ) for the first five resistance coils used in part 1. Those coils were chosen for the graph as they all had the same material and diameter. Since the graphs seemed linear (and that's what theory predicts) a linear fit was applied.

Table 4 contains the resistances measured using a multimeter of the two nichrome resistors used in part 2. ( $R + r$ ) is the resistance, measured using the multimeter, of the nichrome resistor and the wires connecting it to the multimeter.  $r$  is the resistance, measured using the multimeter to be  $0.9 \pm 0.1 \, \Omega$ , of just the wires used for connecting the multimeter to the nichrome resistor.  $R$  is the calculated resistance of the nichrome resistor based on these measurements. These resistance values,  $R_1 = 11.4 \pm 0.1 \, \Omega$  and  $R_2 = 29.7 \pm 0.1 \, \Omega$ , will be referred to as the true values.

Table 5 has the theoretical resistances for part 2.  $R_{1+2}$  is the theoretical equivalent resistance for the two resistors in series.  $R_{1||2}$  is the theoretical equivalent resistance for the two resistors in parallel.

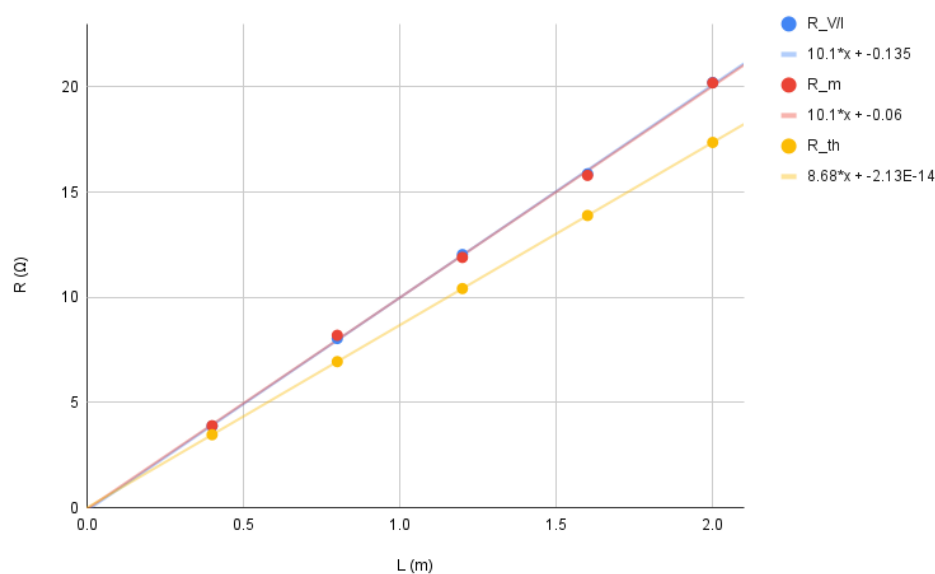

**Figure 1.** Resistance vs Length (Constant  $\rho$  and  $A$ )

**Table 4.** Part 2 True Resistances

Note:  $r$ , the resistance of the two wires connected to the multimeter, was measured to be  $0.9 \pm 0.1 \Omega$ .

	$R + r (\Omega)$	$R (\Omega)$
1	$12.3 \pm 0.1$	$11.4 \pm 0.1$
2	$30.6 \pm 0.1$	$29.7 \pm 0.1$

**Table 5.** Part 2 Theoretical Resistances

	Resistance ( $\Omega$ )
$R_{1+2}$	$41.1 \pm 0.2$
$R_{1  2}$	$8.24 \pm 0.07$

Table 6 contains the values for the circuit with just  $R_1$  connected to the power supply.  $V$  is the voltage across the nichrome resistor.  $I$  is the current through the nichrome resistor.  $R_{V/I}$  is the experimental resistance determined using the measured values for  $V$  and  $I$ .

Table 7 contains the values for the circuit with just  $R_2$  connected to the power supply.  $V$  is the voltage across the nichrome resistor.  $I$  is the current through the nichrome resistor.  $R_{V/I}$  is the experimental resistance determined using the measured values for  $V$  and  $I$ .

Table 8 contains the values for the circuit with  $R_1$  and  $R_2$  connected to the power supply in series.  $V$  is the voltage across both nichrome resistors.  $I$  is the current through both nichrome resistors.  $R_{V/I}$  is the experimental resistance determined using

**Table 6.** Part 2  $R_1$  Experimental Values

$V$ (V)	$I$ (mA)	$R_{V/I}$ ( $\Omega$ )
$0.000 \pm 0.001$	$0.00 \pm 0.01$	undefined
$0.744 \pm 0.001$	$66.8 \pm 0.1$	$11.14 \pm 0.02$
$1.491 \pm 0.001$	$134.0 \pm 0.1$	$11.13 \pm 0.01$
$2.257 \pm 0.001$	$202.8 \pm 0.1$	$11.129 \pm 0.007$
$3.000 \pm 0.001$	$269.6 \pm 0.1$	$11.128 \pm 0.006$

**Table 7.** Part 2  $R_2$  Experimental Values

$V$ (V)	$I$ (mA)	$R_{V/I}$ ( $\Omega$ )
$0.000 \pm 0.001$	$0.00 \pm 0.01$	undefined
$0.746 \pm 0.001$	$24.96 \pm 0.01$	$29.89 \pm 0.04$
$1.500 \pm 0.001$	$50.16 \pm 0.01$	$29.90 \pm 0.02$
$2.255 \pm 0.001$	$75.4 \pm 0.1$	$29.91 \pm 0.04$
$2.998 \pm 0.001$	$100.3 \pm 0.1$	$29.89 \pm 0.03$

the measured values for  $V$  and  $I$ .

**Table 8.** Part 2  $R_{1+2}$  Experimental Values

$V$ (V)	$I$ (mA)	$R_{V/I}$ ( $\Omega$ )
$0.000 \pm 0.001$	$0.00 \pm 0.01$	undefined
$0.757 \pm 0.001$	$18.37 \pm 0.01$	$41.21 \pm 0.06$
$1.496 \pm 0.001$	$36.29 \pm 0.01$	$41.22 \pm 0.03$
$2.254 \pm 0.001$	$54.69 \pm 0.01$	$41.21 \pm 0.02$
$3.001 \pm 0.001$	$72.8 \pm 0.1$	$41.22 \pm 0.06$

Table 9 contains the values for the circuit with  $R_1$  and  $R_2$  connected to the power supply in parallel.  $V$  is the voltage across both nichrome resistors.  $I$  is the current through both nichrome resistors.  $R_{V/I}$  is the experimental resistance determined using the measured values for  $V$  and  $I$ .

**Table 9.** Part 2  $R_{1||2}$  Experimental Values

$V$ (V)	$I$ (mA)	$R_{V/I}$ ( $\Omega$ )
$0.000 \pm 0.001$	$0.00 \pm 0.01$	undefined
$0.749 \pm 0.001$	$91.4 \pm 0.1$	$8.19 \pm 0.01$
$1.502 \pm 0.001$	$183.5 \pm 0.1$	$8.185 \pm 0.007$
$2.252 \pm 0.001$	$275.5 \pm 0.1$	$8.174 \pm 0.005$
$3.000 \pm 0.001$	$367.6 \pm 0.1$	$8.161 \pm 0.004$

Table 10 contains the voltage and current measurements made of the series circuit at 4 V.  $V_1$  is the voltage across resistor 1.  $V_2$  is the voltage across resistor 2.  $V_{1+2}$  is

the voltage across both resistors.  $I_1$  is the current between the resistors, after coming from the power supply and through resistor 1.  $I_2$  is the current after resistor 2, right before reaching the negative terminal of the power supply.  $I_{1+2}$  is the current next to the positive terminal of the power supply, right before reaching the first resistor.

**Table 10.** Part 2 Series Circuit at 4 V

	$V$ (V)	$I$ (mA)
$R_1$	$1.084 \pm 0.001$	$96.5 \pm 0.1$
$R_2$	$2.915 \pm 0.001$	$97.1 \pm 0.1$
$R_{1+2}$	$4.002 \pm 0.001$	$97.1 \pm 0.1$

Table 11 contains the voltage and current measurements made of the parallel circuit at 4 V.  $V_1$  is the voltage across resistor 1.  $V_2$  is the voltage across resistor 2.  $V_{1||2}$  is the voltage across both resistors.  $I_1$  is the current through resistor 1.  $I_2$  is the current through resistor 2.  $I_{1||2}$  is the current next to the positive terminal of the power supply, right before reaching the junction connected to the two resistors.

**Table 11.** Part 2 Parallel Circuit at 4 V

	$V$ (V)	$I$ (mA)
$R_1$	$3.968 \pm 0.001$	$410.4 \pm 0.1$
$R_2$	$3.927 \pm 0.001$	$155.6 \pm 0.1$
$R_{1  2}$	$4.002 \pm 0.001$	$491.7 \pm 0.1$

### 3. Uncertainty

All the voltage, current, and resistance measurements in the experiment were made using a multimeter. If there were fluctuations in a particular reading with the multimeter (voltage, current, or resistance), then the uncertainty was taken to be the magnitude of the fluctuations, as that gives an upper bound for how much the value could have varied. If the reading with the multimeter (voltage, current, or resistance) was stable and did not fluctuate, then the uncertainty was taken to be the smallest increment of measure, since that was the limiting precision of the equipment.

In parts 1 and 2,  $R_{V/I}$  was calculated using equation 1.

$$R_{V/I} = \frac{V}{I} \quad (1)$$

The uncertainty of  $R_{V/I}$  is given by equation 2.

$$\begin{aligned} \Delta R_{V/I} &= \left[ \left( \frac{\partial R_{V/I}}{\partial V} \Delta V \right)^2 + \left( \frac{\partial R_{V/I}}{\partial I} \Delta I \right)^2 \right]^{\frac{1}{2}} \\ &= \frac{V}{I} \left[ \left( \frac{\Delta V}{V} \right)^2 + \left( \frac{\Delta I}{I} \right)^2 \right]^{\frac{1}{2}} \end{aligned} \quad (2)$$

In part 1,  $R_m$  was calculated using equation 3. Note that the combined value  $(R_m + r)$  was measured, as was the value for  $r$ . But  $R_m$  was not measured, hence why it is being calculated as a difference of two values.

$$R_m = (R_m + r) - r \quad (3)$$

The uncertainty of  $R_m$  is given by equation 4.

$$\begin{aligned} \Delta R_m &= \left[ \left( \frac{\partial R_m}{\partial (R_m + r)} \Delta (R_m + r) \right)^2 + \left( \frac{\partial R_m}{\partial r} \Delta r \right)^2 \right]^{\frac{1}{2}} \\ &= \left[ (\Delta (R_m + r))^2 + (\Delta r)^2 \right]^{\frac{1}{2}} \end{aligned} \quad (4)$$

Similarly in part 2, the true resistance values  $R_1$  and  $R_2$ , referred to as just  $R$ , were calculated using equation 5. Note that the combined value  $(R + r)$  was measured, as was the value for  $r$ . But  $R$  was not measured, hence why it is being calculated as a difference of two values.

$$R = (R + r) - r \quad (5)$$

The uncertainty of  $R$  is given by equation 6.

$$\begin{aligned} \Delta R &= \left[ \left( \frac{\partial R}{\partial (R + r)} \Delta (R + r) \right)^2 + \left( \frac{\partial R}{\partial r} \Delta r \right)^2 \right]^{\frac{1}{2}} \\ &= \left[ (\Delta (R + r))^2 + (\Delta r)^2 \right]^{\frac{1}{2}} \end{aligned} \quad (6)$$

In part 1,  $R_{th}$  was calculated using equation 7.

$$\begin{aligned} R_{th} &= \frac{\rho L}{A} \\ &= \frac{\rho L}{\pi (D/2)^2} \\ &= \frac{4\rho L}{\pi D^2} \end{aligned} \quad (7)$$

Note that the values for  $\rho$ ,  $L$ , and  $D$  were assumed to be exact, without uncertainty. Thus,  $R_{th}$  would have no uncertainty as well.

In part 2,  $R_{1+2}$ , the theoretical resistance for the two resistors in series, was calculated using equation 8.

$$R_{1+2} = R_1 + R_2 \quad (8)$$

The uncertainty of  $R_{1+2}$  is given by equation 9.

$$\begin{aligned} \Delta R_{1+2} &= \left[ \left( \frac{\partial R_{1+2}}{\partial R_1} \Delta R_1 \right)^2 + \left( \frac{\partial R_{1+2}}{\partial R_2} \Delta R_2 \right)^2 \right]^{\frac{1}{2}} \\ &= \left[ (\Delta R_1)^2 + (\Delta R_2)^2 \right]^{\frac{1}{2}} \end{aligned} \quad (9)$$

In part 2,  $R_{1||2}$ , the theoretical resistance for the two resistors in parallel, was calculated using equation 10.

$$R_{1||2} = (R_1^{-1} + R_2^{-1})^{-1} \quad (10)$$

The uncertainty of  $R_{1||2}$  is given by equation 11.

$$\begin{aligned} \Delta R_{1||2} &= \left[ \left( \frac{\partial R_{1||2}}{\partial R_1} \Delta R_1 \right)^2 + \left( \frac{\partial R_{1||2}}{\partial R_2} \Delta R_2 \right)^2 \right]^{\frac{1}{2}} \\ &= \left[ \left( [R_1^{-1} + R_2^{-1}]^{-2} \frac{\Delta R_1}{R_1^2} \right)^2 + \left( [R_1^{-1} + R_2^{-1}]^{-2} \frac{\Delta R_2}{R_2^2} \right)^2 \right]^{\frac{1}{2}} \end{aligned} \quad (11)$$

#### 4. Conclusion

In part 1, the resistances of 7 different resistance coils were determined using three different techniques. Descriptions of the coils are in table 1, and the calculated resistance values are in table 3. The experimental resistances  $R_{V/I}$  and  $R_m$  had similar values for all the coils. Coils 1, 4, and 5 had resistance values that overlapped within uncertainty, while the rest of the coils (2, 3, 6, and 7) had values that were still fairly close and almost within uncertainty. While the experimental resistances were similar, their values were all higher than the corresponding theoretical resistances  $R_{th}$ . One possible explanation is that when measuring voltage and resistance, the multimeter was connected to the resistance coils through a small bit of copper wire. This copper wire section was not included when measuring  $r$ , but it was included when measuring  $(R_m + r)$ . As a result, this would cause  $R_m$  to be higher than expected. This extra resistance would also have increased the measured value for  $V$ , thereby causing  $R_{V/I}$  to be higher than expected. Another possibility is that the temperature of the room did not match the reference temperature of 20 °C. The table the resistivity values were taken from used a reference temperature of 20 °C. If the room were warmer than 20 °C, then the actual resistivity values would have been slightly higher than the  $\rho$  values used for calculations. This would cause  $R_{th}$  to be lower than expected.

Resistance coils 1 through 5 were all made of the same material and had the same cross-sectional area, but they had different lengths. Figure 1 plots resistance ( $R_{V/I}$ ,  $R_m$ , and  $R_{th}$ ) versus length ( $L$ ). The graphs are linear with y-intercepts close to zero. Thus, the data indicates that the resistance of a wire/coil is proportional to its length.

Resistance coils 5 and 6 were made of the same material and had the same length, but they had different cross-sectional areas. The experimental resistances for coil 5 ( $R_{V/I} = 20.21 \pm 0.03 \, \Omega$ ,  $R_m = 20.2 \pm 0.1 \, \Omega$ ) were higher than the experimental resistances for coil 6 ( $R_{V/I} = 11.84 \pm 0.02 \, \Omega$ ,  $R_m = 11.6 \pm 0.1 \, \Omega$ ). The cross-sectional area of coil 5 ( $A = \frac{1}{4}\pi(0.0254 \, \text{cm})^2 = 5.07 \times 10^{-4} \, \text{cm}^2$ ) was lower than the cross-sectional area of coil 6 ( $A = \frac{1}{4}\pi(0.0320 \, \text{cm})^2 = 8.04 \times 10^{-4} \, \text{cm}^2$ ). Thus, the data suggests that as cross-sectional area increases, resistances decreases.



Resistance coil 7, made out of copper, was 10 times longer than coil 5, made out of nickel-silver, with the same cross-sectional area. Since it has already been shown that resistance is proportional to length, then dividing the experimental resistance values for coil 7 by 10 would allow us to compare the resistances of two wires of identical dimensions but different materials. Thus, our hypothetical 200 cm long copper resistance coil of diameter 0.0254 cm would have experimental resistances  $R_{V/I} = 0.696 \pm 0.002 \, \Omega$  and  $R_m = 0.72 \pm 0.01 \, \Omega$ . For comparison, coil 5 had experimental resistances  $R_{V/I} = 20.21 \pm 0.03 \, \Omega$  and  $R_m = 20.2 \pm 0.1 \, \Omega$ . The resistance of coil 5 was much higher than the resistance of the hypothetical copper wire with identical length and diameter. This supports the idea that resistance depends on material, with some materials having more resistance for a given wire shape than others.

In part 2, the resistance of two nichrome coils were measured, and those measurements were used to determine the resistance of four different circuits. The true values for both resistors are in table 4, the experimental values of the first coil are in table 6, and the experimental values of the second coil are in table 7. For resistor 1, the experimental resistances  $R_{V/I}$  were within uncertainty of each other and had a mean of  $11.13 \, \Omega$ . This resistance value is about  $0.3 \, \Omega$  lower than the true value of  $R_1 = 11.4 \pm 0.1 \, \Omega$ , a difference larger than the uncertainty. One possible explanation is that the alligator clips from the multimeter were not connected to ends of the resistor in the exact same spot each time. The ends of the nichrome resistor had bits of free wire that were not wrapped around the dowel. The multimeter wires were clipped to those free ends, but care was not taken to make sure that the clips were connected to the same location each time. When measuring the voltage, the clips may have been connected slightly closer together than when measuring the resistance. As a result, the voltage drop measured would be for a slightly smaller length of resistor, and would thus be lower than expected. A smaller voltage measurement would lead to a smaller calculated resistance. For resistor 2, the experimental resistances  $R_{V/I}$  were within uncertainty of each other and had a mean of  $29.90 \, \Omega$ . This resistance value is about  $0.2 \, \Omega$  higher than the true value of  $R_2 = 29.7 \pm 0.1 \, \Omega$ , a difference larger than the uncertainty. One possible explanation is that the alligator clips from the multimeter were not connected to ends of the resistor in the exact same spot each time. When measuring the voltage, the clips may have been connected slightly further apart than when measuring the resistance. As a result, the voltage drop measured would be for a slightly larger length of resistor, and would thus be higher than expected. A higher voltage measurement would lead to a higher calculated resistance.

After measuring the resistance of the first two circuits containing only one of the nichrome coils at a time, both coils were connected in series, then in parallel. The theoretical resistances of these two circuits are in table 5, the experimental equivalent resistance values of the series circuit are in table 8, and the experimental equivalent resistance values of the parallel circuit are in table 9. For the series circuit, the experimental resistances  $R_{V/I}$  were within uncertainty of each other and had a mean of  $41.22 \, \Omega$ . This resistance value is about  $0.1 \, \Omega$  higher than the theoretical value of

$R_{1+2} = 41.1 \pm 0.2 \, \Omega$ , a difference smaller than the uncertainty. Thus, the result agrees with theory within uncertainty. For the parallel circuit, the experimental resistances  $R_{V/I}$  were within uncertainty of each other, or at least very close to matching within uncertainty, and had a mean of  $8.18 \, \Omega$ . This resistance value is about  $0.06 \, \Omega$  lower than the theoretical value of  $R_{1||2} = 8.24 \pm 0.07 \, \Omega$ , a difference smaller than the uncertainty. Thus, the result agrees with theory within uncertainty.

Measurements of voltage and current were made of the series and parallel circuits at 4 V. The results for the two resistors in series are in table 10, and the results for the two resistors in parallel are in table 11. Focusing on the series circuit, the voltage across resistor 1 was  $V_1 = 1.084 \pm 0.001 \, \text{V}$ , the voltage across resistor 2 was  $V_2 = 1.084 \pm 0.001 \, \text{V}$ , and the voltage across both resistors was  $V_{1+2} = 4.002 \pm 0.001 \, \text{V}$ . Resistor 2 had a larger voltage than resistor 1, which is consistent with what theory predicts for resistors in series. Since resistors in series have the same current  $I$ , and  $V = IR$ , a larger resistance  $R$  leads to a larger voltage  $V$ . The sum  $V_1 + V_2 = 3.999 \pm 0.001 \, \text{V}$  is approximately equal to  $V_{1+2}$ , only about  $0.003 \, \text{V}$  lower and just barely larger than the uncertainty. In theory,  $V_1 + V_2 = V_{1+2}$  since voltages add together when traversing a section of a circuit, and the results got very close to demonstrating this. This small discrepancy is possibly due to the multimeter clips being connected to the resistors in such a way that a small section of resistor was skipped over in the separate measurements for  $V_1$  and  $V_2$ , a section which was included in the overall measurement for  $V_{1+2}$ . Turning to the current measurements, the current between the resistors was  $I_1 = 96.5 \pm 0.1 \, \text{mA}$ , the current after the second resistor was  $I_2 = 97.1 \pm 0.1 \, \text{mA}$ , and the current next to the power supply was  $I_{1+2} = 97.1 \pm 0.1 \, \text{mA}$ . In theory, each of these current measurements should be identical since components connected in series have the same current.  $I_2$  and  $I_{1+2}$  had identical values, but  $I_1$  was about  $0.6 \, \text{mA}$  lower. One potential explanation is that when measuring  $I_2$  and  $I_{1+2}$ , no extra wires needed to be added to the circuit; the components were simply rearranged. But to measure  $I_1$ , an extra wire needed to be added in order to connect the multimeter between the resistors. This extra wire would have increased the total resistance of the series circuit, thereby decreasing the measured current.

## 5. Citations

- [1] Karen Schnurbusch, *Physics 4B Lab Book*, Mt. San Antonio College, 2023, pp. 65-70.
- [2] Karen Schnurbusch, *Physics 4B Equations*, Mt. San Antonio College, 2023, pp. 4, 10.