

# Circuits Lab

**Vincent Edwards**

Mt. San Antonio College, Physics 4B, CRN 42240  
May 8, 2023

$$R_2 = 40 \, \Omega$$


## 1. Purpose

The goal of the exercise was to use Kirchhoff's rules to analyze 7 different circuits and calculate current, voltage, and power for each circuit element. For the first 4 circuits, the voltage and current calculations were compared to results obtained using an online circuit simulator. In each case, the voltage across a resistor was calculated with  $V = IR$ , and the power dissipated by a circuit element with  $P = VI$ .

## 2. Results

The following tables contain the theoretical voltage, current, and power for each circuit element for each of the 7 circuits. In addition, there is an annotated circuit diagram for each circuit.

### 2.1. Circuit 1

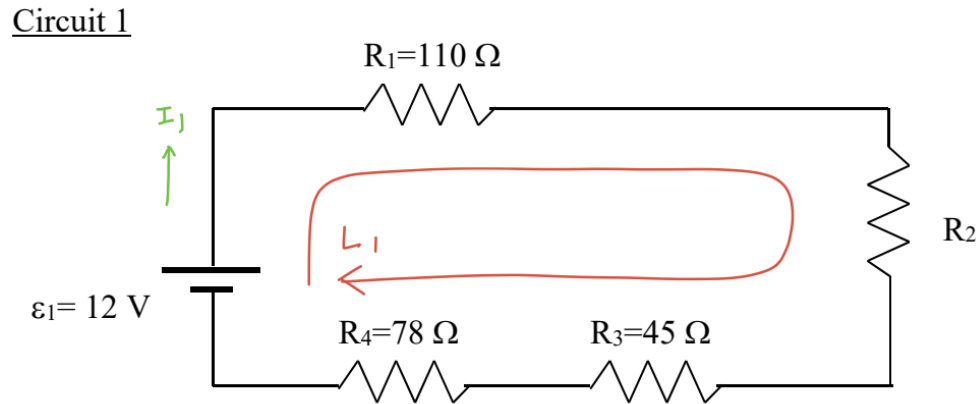

**Figure 1.** Circuit 1

**Table 1.** Circuit 1  $V$ ,  $I$ , and  $P$

|                 | $V$ (V) | $I$ (A) | $P$ (W) |
|-----------------|---------|---------|---------|
| $\mathcal{E}_1$ | 12.0    | 0.0440  | 0.527   |
| $R_1$           | 4.84    | 0.0440  | 0.213   |
| $R_2$           | 1.76    | 0.0440  | 0.0773  |
| $R_3$           | 1.98    | 0.0440  | 0.0869  |
| $R_4$           | 3.43    | 0.0440  | 0.151   |

$$L_1 : \mathcal{E}_1 - I_1 R_1 - I_1 R_2 - I_1 R_3 - I_1 R_4 = 0$$

$$I_1 = \frac{\mathcal{E}_1}{R_1 + R_2 + R_3 + R_4}$$

$$I_1 = 0.0440\text{ A}$$

## 2.2. Circuit 2

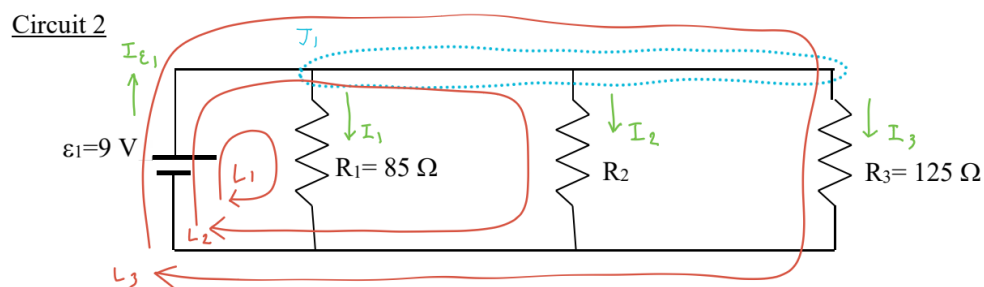


Figure 2. Circuit 2

Table 2. Circuit 2  $V$ ,  $I$ , and  $P$ 

|                 | $V$ (V) | $I$ (A) | $P$ (W) |
|-----------------|---------|---------|---------|
| $\mathcal{E}_1$ | 9.00    | 0.403   | 3.63    |
| $R_1$           | 9.00    | 0.106   | 0.953   |
| $R_2$           | 9.00    | 0.225   | 2.02    |
| $R_3$           | 9.00    | 0.0720  | 0.648   |

## 2.3. Circuit 3

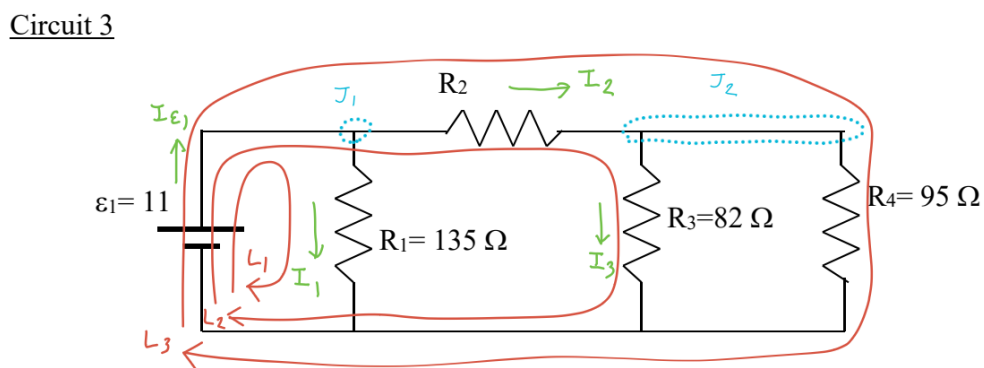
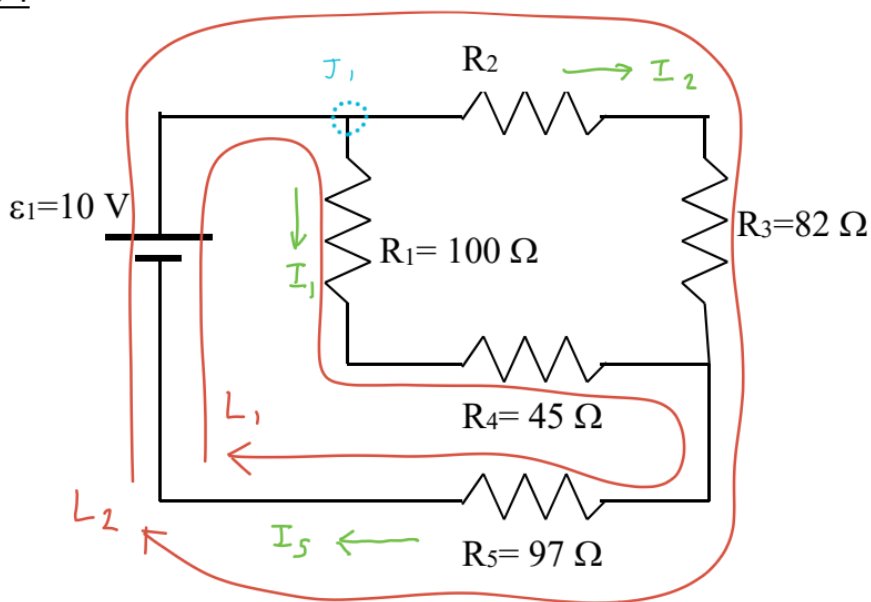


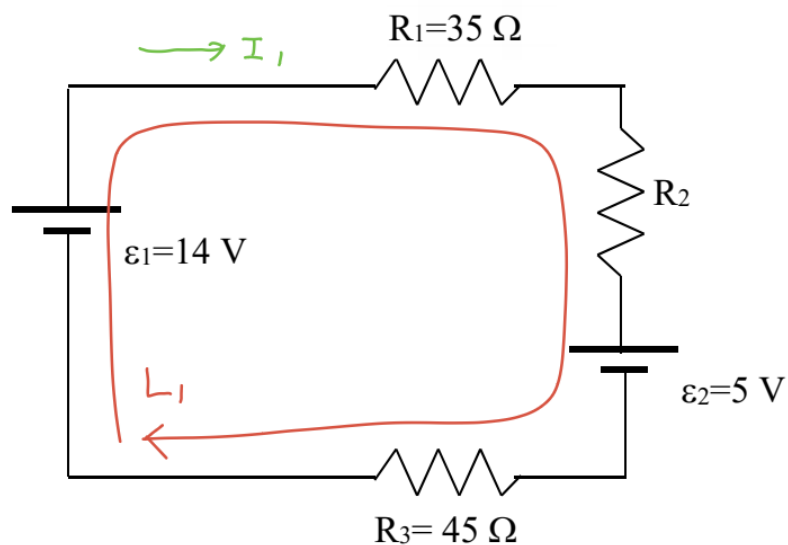
Figure 3. Circuit 3

**Table 3.** Circuit 3  $V$ ,  $I$ , and  $P$ 


|                 | $V$ (V) | $I$ (A) | $P$ (W) |
|-----------------|---------|---------|---------|
| $\mathcal{E}_1$ | 11.0    | 0.212   | 2.34    |
| $R_1$           | 11.0    | 0.0815  | 0.896   |
| $R_2$           | 5.24    | 0.131   | 0.686   |
| $R_3$           | 5.76    | 0.0703  | 0.405   |
| $R_4$           | 5.76    | 0.0607  | 0.350   |

**Circuit 4****Figure 4.** Circuit 4**Table 4.** Circuit 4  $V$ ,  $I$ , and  $P$ 

|                 | $V$ (V) | $I$ (A) | $P$ (W) |
|-----------------|---------|---------|---------|
| $\mathcal{E}_1$ | 10.0    | 0.0613  | 0.613   |
| $R_1$           | 2.80    | 0.0280  | 0.0783  |
| $R_2$           | 1.33    | 0.0333  | 0.0443  |
| $R_3$           | 2.73    | 0.0333  | 0.0907  |
| $R_4$           | 1.26    | 0.0280  | 0.0353  |
| $R_5$           | 5.94    | 0.0613  | 0.364   |


Circuit 5**Figure 5.** Circuit 5**Table 5.** Circuit 5  $V$ ,  $I$ , and  $P$ 

|                 | $V$ (V) | $I$ (A) | $P$ (W) |
|-----------------|---------|---------|---------|
| $\mathcal{E}_1$ | 14.0    | 0.0750  | 1.05    |
| $\mathcal{E}_2$ | 5.00    | 0.0750  | 0.375   |
| $R_1$           | 2.62    | 0.0750  | 0.197   |
| $R_2$           | 3.00    | 0.0750  | 0.225   |
| $R_3$           | 3.38    | 0.0750  | 0.253   |

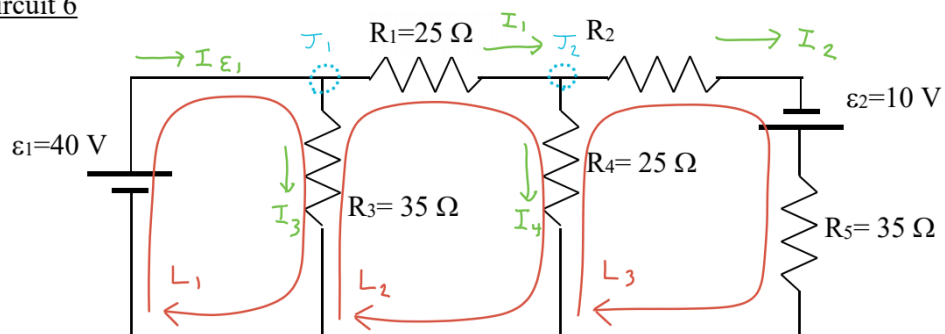Circuit 6**Figure 6.** Circuit 6

**Table 6.** Circuit 6  $V$ ,  $I$ , and  $P$ 

|                 | $V$ (V) | $I$ (A) | $P$ (W) |
|-----------------|---------|---------|---------|
| $\mathcal{E}_1$ | 40.0    | 2.11    | 84.6    |
| $\mathcal{E}_2$ | 10.0    | 0.343   | 3.43    |
| $R_1$           | 24.3    | 0.971   | 23.6    |
| $R_2$           | 13.7    | 0.343   | 4.70    |
| $R_3$           | 40.0    | 1.14    | 45.7    |
| $R_4$           | 15.7    | 0.629   | 9.88    |
| $R_5$           | 12.0    | 0.343   | 4.11    |

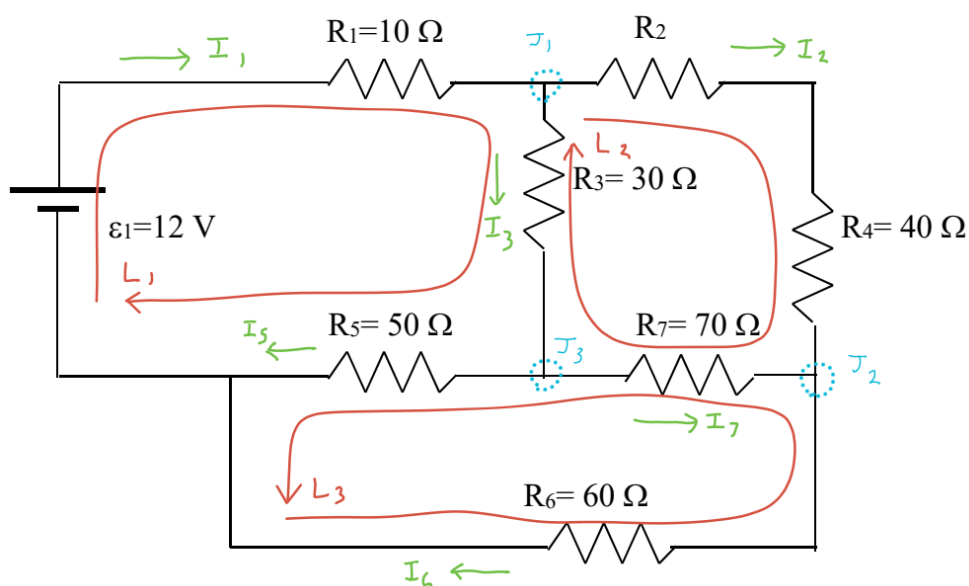**Circuit 7** (It is recommended to solve this circuit using a matrix.)**Figure 7.** Circuit 7**Table 7.** Circuit 7  $V$ ,  $I$ , and  $P$ 

|                 | $V$ (V) | $I$ (A) | $P$ (W) |
|-----------------|---------|---------|---------|
| $\mathcal{E}_1$ | 12.0    | 0.200   | 2.40    |
| $R_1$           | 2.00    | 0.200   | 0.399   |
| $R_2$           | 2.58    | 0.0646  | 0.167   |
| $R_3$           | 4.05    | 0.135   | 0.547   |
| $R_4$           | 2.58    | 0.0646  | 0.167   |
| $R_5$           | 5.95    | 0.119   | 0.709   |
| $R_6$           | 4.83    | 0.0806  | 0.390   |
| $R_7$           | 1.12    | 0.0160  | 0.0179  |

*2.4. Circuit 4*

*2.5. Circuit 5*

*2.6. Circuit 6*

*2.7. Circuit 7*

### **3. Conclusion**

### **4. Citations**

- [1] Karen Schnurbusch, *Physics 4B Lab Book*, Mt. San Antonio College, 2023, pp. 71-74.
- [2] Karen Schnurbusch, *Physics 4B Equations*, Mt. San Antonio College, 2023, pp. 4, 5.